

Application Notes: Integrating the JX040 SCR into Microcontroller-Based Power Electronics Projects

Author: BenchChem Technical Support Team. **Date:** December 2025

Compound of Interest

Compound Name: JX040

Cat. No.: B608285

[Get Quote](#)

1. Introduction

The **JX040** is a sensitive gate Silicon Controlled Rectifier (SCR) capable of controlling significant power in AC circuits.[1][2] Its high dv/dt rate and strong resistance to electromagnetic interference make it a robust choice for various power control applications.[1] [2] These application notes provide a detailed guide for integrating the **JX040** into microcontroller-based projects, specifically focusing on AC phase angle control for power regulation. The protocols and methodologies are intended for researchers and engineers in the field of power electronics.

2. JX040 Key Electrical Characteristics


The following table summarizes the essential electrical characteristics of the **JX040** SCR, as derived from its datasheet.[2][3][4] These parameters are critical for circuit design and ensuring reliable operation within safe limits.

Parameter	Symbol	Value	Unit
Repetitive Peak Off-State Voltage	VDRM	600	V
Repetitive Peak Reverse Voltage	VRRM	600	V
RMS On-State Current	IT(RMS)	4	A
Non-Repetitive Surge Peak On-State Current	ITSM	30	A
Gate Trigger Current	IGT	≤200	μA
Gate Trigger Voltage	VGT	0.6 - 0.8	V
Holding Current	IH	5	mA
Latching Current	IL	6	mA
Critical Rate of Rise of On-State Current	di/dt	50	A/μs
Operating Junction Temperature Range	Tj	-40 to 110	°C

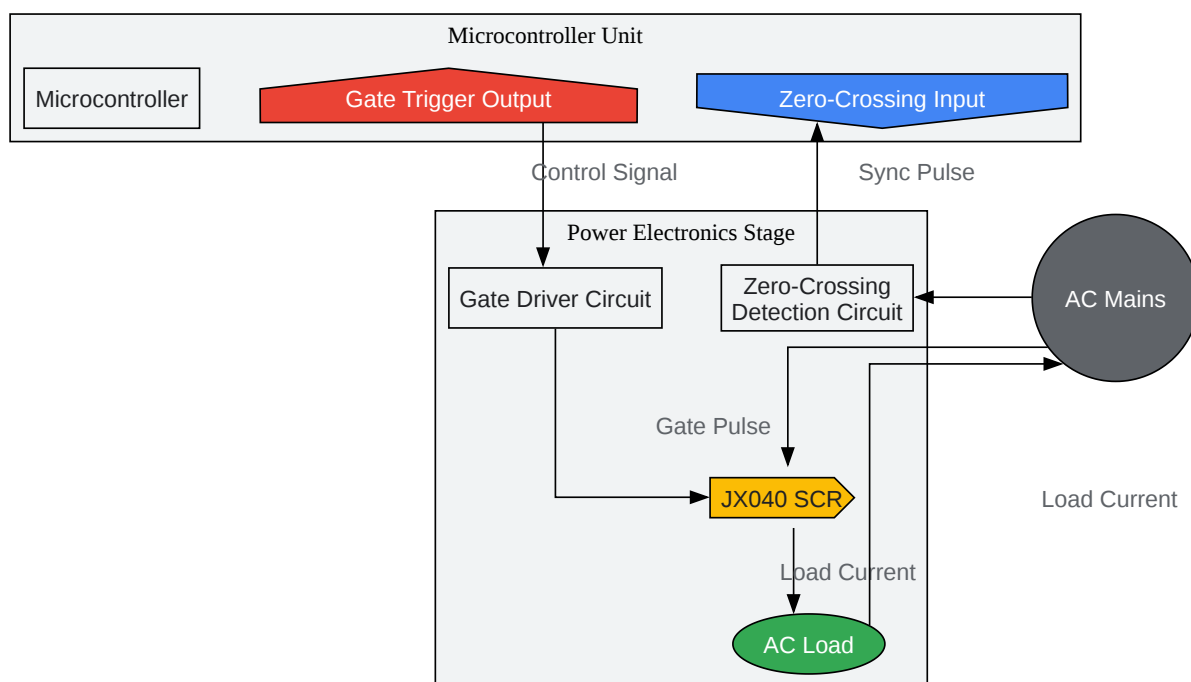3. System Architecture and Signaling Pathways

A fundamental application of the **JX040** in microcontroller-based systems is AC phase angle control. This technique allows for the precise control of power delivered to an AC load, such as a heating element or a universal motor. The core principle is to trigger the SCR at a specific point (phase angle) in each AC cycle.


A block diagram of the system is presented below, illustrating the relationship between the microcontroller, the zero-crossing detection circuit, the **JX040** gate driver, and the AC load.



[Click to download full resolution via product page](#)

Figure 1: System architecture for AC phase angle control.

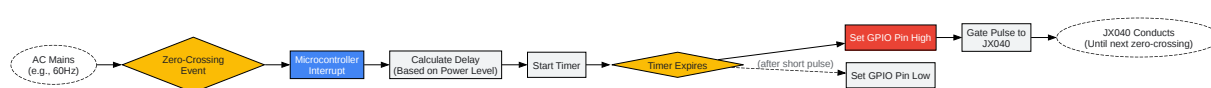The signaling pathway for triggering the **JX040** is initiated by the zero-crossing detection circuit, which provides a synchronization pulse to the microcontroller at the beginning of each AC half-cycle. The microcontroller then waits for a calculated delay before sending a trigger pulse to the gate driver circuit, which in turn activates the **JX040**.



[Click to download full resolution via product page](#)

*Figure 2: Signaling pathway for **JX040** gate triggering.*

4. Experimental Protocols

The following protocols outline the procedures for setting up and testing the **JX040** in an AC phase angle control circuit.

4.1. Protocol 1: Zero-Crossing Detector Verification

Objective: To verify the correct operation of the zero-crossing detection circuit.

Materials:

- Oscilloscope
- Function generator (for safe low-voltage testing) or Step-down transformer
- Constructed zero-crossing detection circuit

Procedure:

- Disconnect the microcontroller and **JX040** from the circuit.
- Apply a low-voltage AC signal (e.g., 12V AC) to the input of the zero-crossing detector.
- Connect one oscilloscope probe to the AC input and another to the output of the zero-crossing detector.

- Observe the waveforms. The output should be a sharp pulse that aligns with the zero-voltage points of the input AC waveform.
- Measure the width of the output pulse.
- Record the alignment and pulse width.

4.2. Protocol 2: **JX040** Gate Triggering and Power Control

Objective: To test the microcontroller's ability to trigger the **JX040** and control the power delivered to a resistive load.

Materials:

- Assembled system as per Figure 1 (with a resistive load, e.g., an incandescent lamp)
- Oscilloscope with current probe
- Microcontroller development board with appropriate firmware
- Isolated power supply for the microcontroller

Procedure:


- Ensure the microcontroller is programmed to generate a gate trigger pulse at a fixed delay after the zero-crossing interrupt.
- Connect an oscilloscope probe across the AC load to measure the voltage.
- Use a current probe to measure the current flowing through the load.
- Power on the microcontroller and then the main AC supply to the power stage.
- Observe the load voltage waveform. It should be a chopped sine wave, indicating that the SCR is turning on at a specific phase angle.
- Vary the trigger delay in the microcontroller's firmware and observe the corresponding change in the load's brightness (if using a lamp) and the shape of the voltage/current

waveforms.

- Capture waveforms for different delay settings (e.g., corresponding to 25%, 50%, and 75% power).
- Measure the RMS voltage and current for each setting.

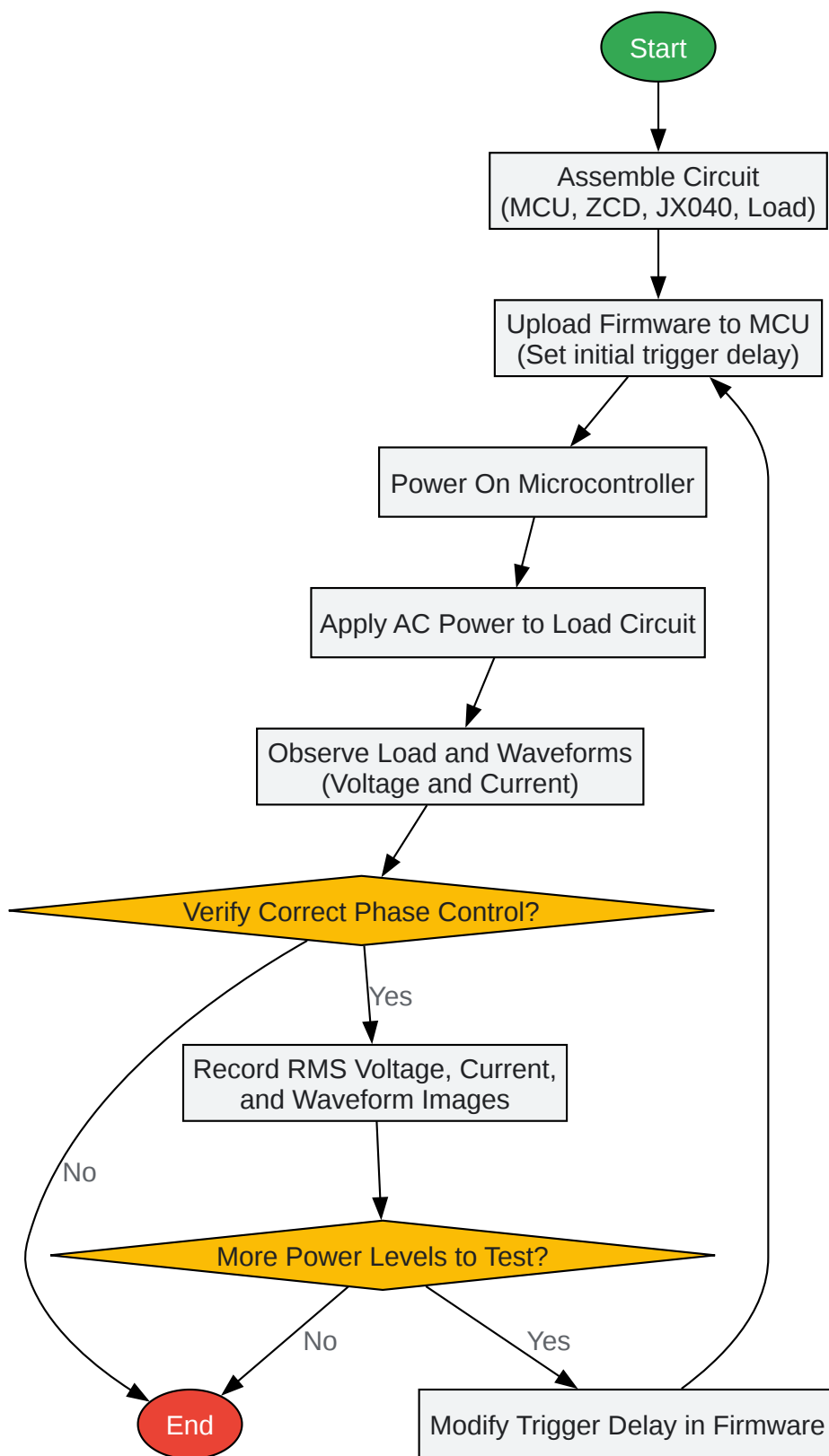5. Experimental Workflow

The following diagram outlines the logical workflow for conducting the power control experiment.



[Click to download full resolution via product page](#)

Figure 3: Experimental workflow for power control characterization.

6. Safety Precautions

- The circuits described operate at mains voltage, which is lethal. Ensure all power is disconnected before making any adjustments to the circuit.
- Use an isolation transformer for the power stage during testing and development.
- The **JX040** may require a heat sink, especially when operating at higher currents.
- Always wear appropriate personal protective equipment (PPE), including safety glasses.

By following these application notes and protocols, researchers and engineers can effectively integrate the **JX040** SCR into microcontroller-based power electronics projects for precise AC power control.

Need Custom Synthesis?

BenchChem offers custom synthesis for rare earth carbides and specific isotopic labeling.

Email: info@benchchem.com or [Request Quote Online](#).

References

- 1. datasheet4u.com [datasheet4u.com]
- 2. surgecomponents.com [surgecomponents.com]
- 3. JX040 pdf, JX040 Download, JX040 Description, JX040 Datasheet, JX040 view ::: ALLDATASHEET ::: [pdfapp.alldatasheet.com]
- 4. JX040 Datasheet(PDF) - JIEJIE MICROELECTRONICS CO.,Ltd [alldatasheet.com]
- To cite this document: BenchChem. [Application Notes: Integrating the JX040 SCR into Microcontroller-Based Power Electronics Projects]. BenchChem, [2025]. [Online PDF]. Available at: [<https://www.benchchem.com/product/b608285#integrating-jx040-into-microcontroller-based-power-electronics-projects>]

Disclaimer & Data Validity:

The information provided in this document is for Research Use Only (RUO) and is strictly not intended for diagnostic or therapeutic procedures. While BenchChem strives to provide accurate protocols, we make no warranties, express or implied, regarding the fitness of this product for every specific experimental setup.

Technical Support: The protocols provided are for reference purposes. Unsure if this reagent suits your experiment? [[Contact our Ph.D. Support Team for a compatibility check](#)]

Need Industrial/Bulk Grade? [Request Custom Synthesis Quote](#)

BenchChem

Our mission is to be the trusted global source of essential and advanced chemicals, empowering scientists and researchers to drive progress in science and industry.

Contact

Address: 3281 E Guasti Rd

Ontario, CA 91761, United States

Phone: (601) 213-4426

Email: info@benchchem.com